

1. A list of all the electronic components that will be soldered to your PCB

Microcontroller

XIAO-ESP32-C3

Touch capacitor

CAP1188-1-CP-TR

Heart rate sensor

MAX30102

Battery Cell

BT1 Single-cell battery

Switch

SW_DPST_x2

2. A screenshot of your circuit in the Schematic Editor window of KiCad

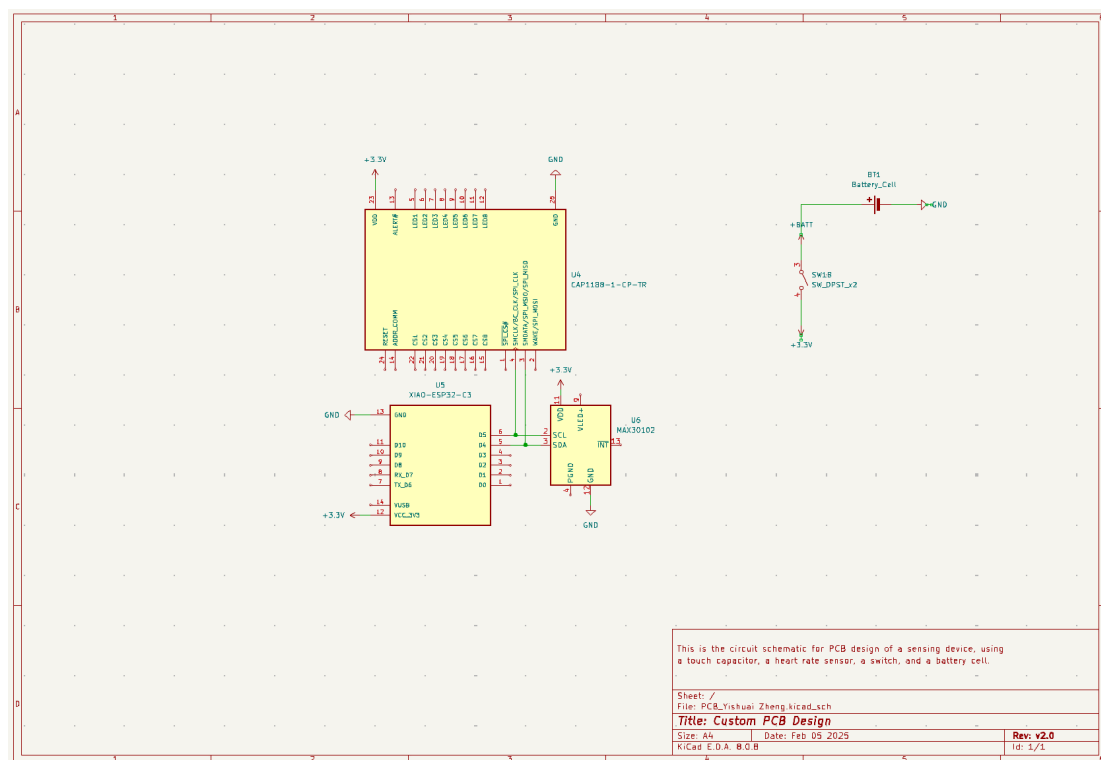


Figure 1.1 Schematic Editor Circuit in KiCAD

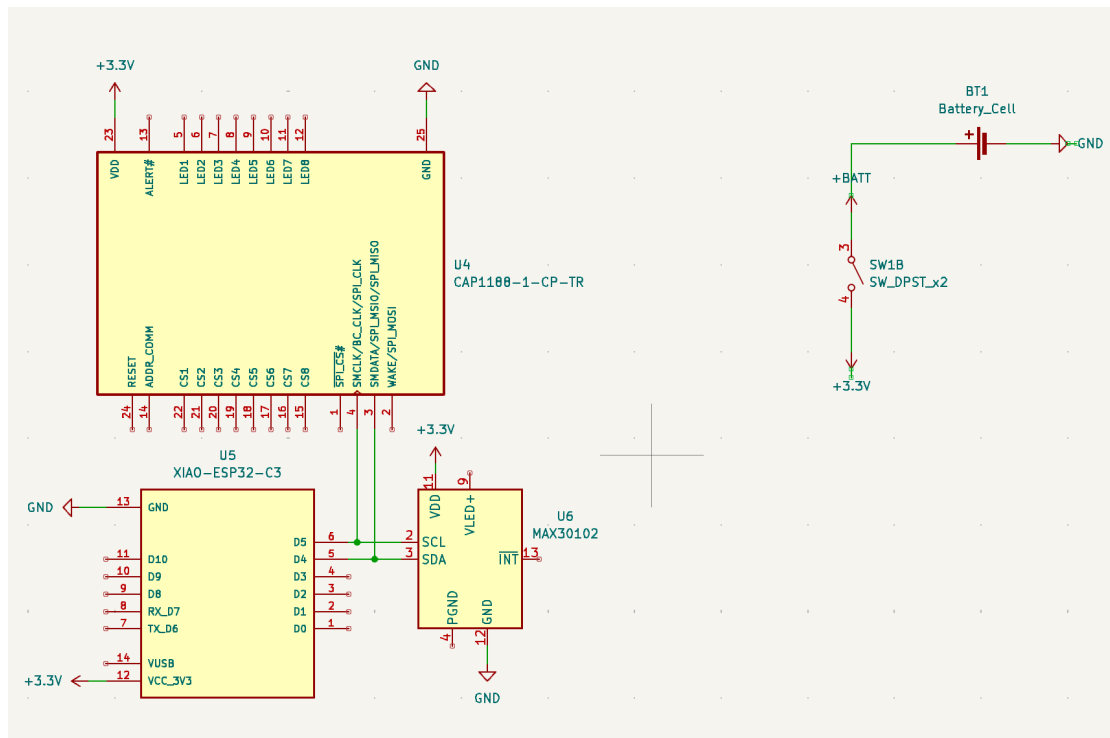


Figure 1.2 Schematic Editor Circuit in KiCAD (Zoom in)

I didn't use any resistors and capacitors as all the sensors and microcontroller in my device keep as 3.3V typ.

3. A screenshot of your circuit board in the PCB Editor window of KiCad

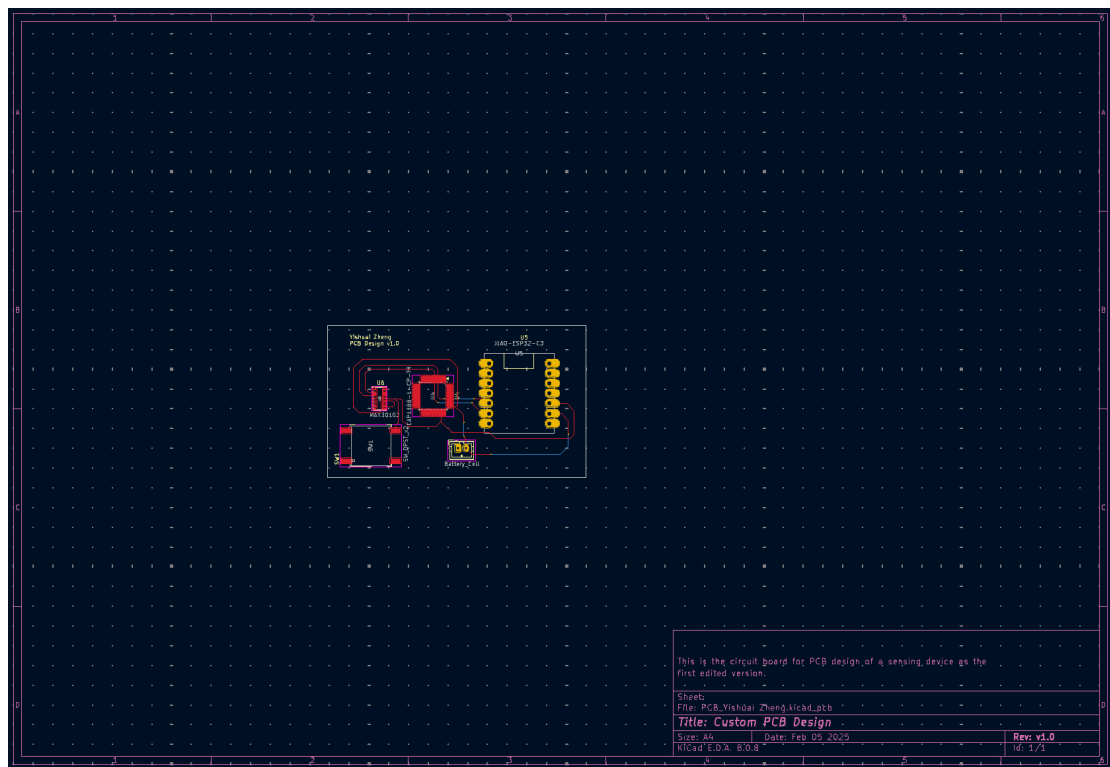


Figure 2.1 PCB Editor Circuit Board in KiCAD

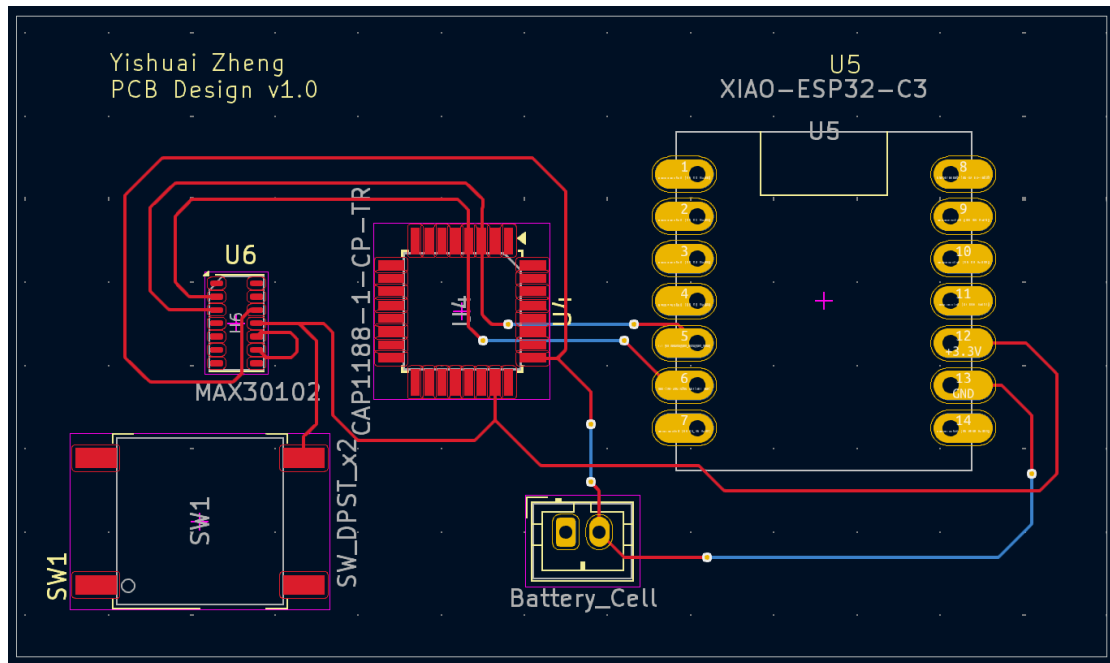


Figure 2.2 PCB Editor Circuit Board in KiCAD (Zoom in)

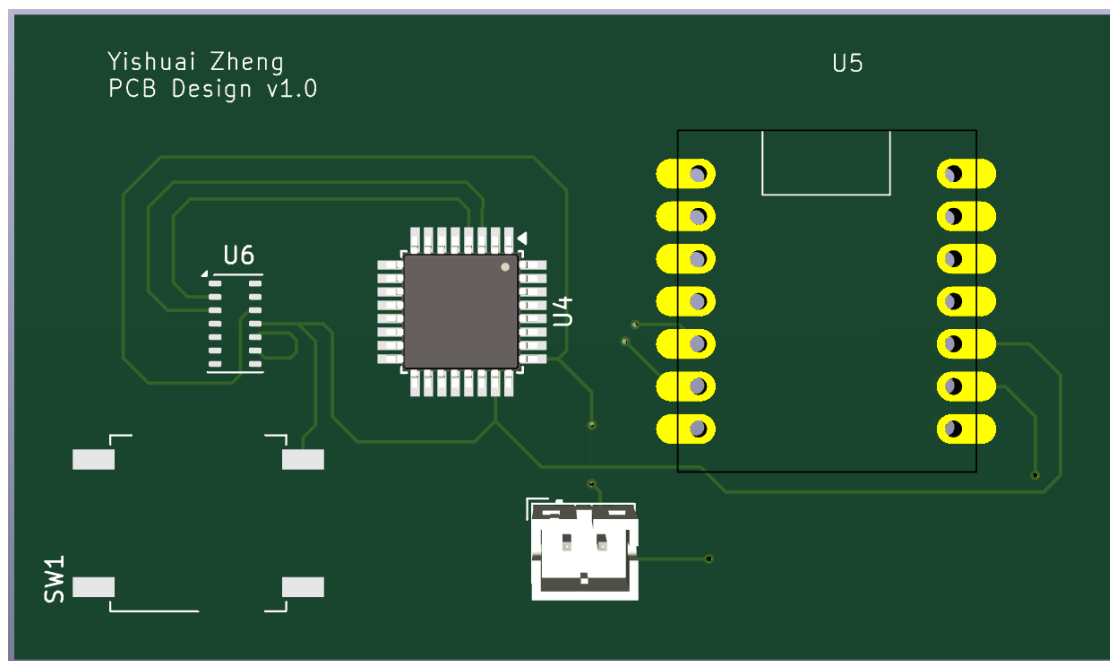


Figure 2.3 PCB Editor Circuit Board in KiCAD (3D View)